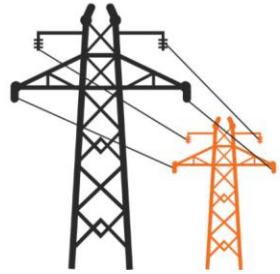


Motivation of today

Single wire equivalent diagram



Question of the day:
**How these
devices work ?**